 


```

1  `timescale 1ns / 1ns // `timescale time_unit/time_precision
2
3  module sequence_detector(input [9:0] SW, input [0:0] KEY, output [9:0] LEDR);
4
5      wire w, clock, resetn, out_light;
6      // y_Q represents current state, Y_D represents next state
7      reg [3:0] y_Q, Y_D;
8      localparam A = 4'b0000, B = 4'b0001, C = 4'b0010, D = 4'b0011,
9                  E = 4'b0100, F = 4'b0101, G = 4'b0110;
10
11      /*
12       * SW[0] reset when 0
13       * SW[1] input signal
14       * KEY[0] clock signal
15       * LEDR[3:0] displays current state
16       * LEDR[9] displays output
17      */
18
19      assign w = SW[1];
20      assign clock = ~KEY[0];
21      assign resetn = SW[0];
22
23      always@(*) // state table
24      begin
25          // logic for state transitions
26          case (y_Q)
27              A: begin
28                  if (~w) Y_D = A;
29                  else Y_D = B;
30              end
31              B: begin
32                  if (~w) Y_D = A;
33                  else Y_D = C;
34              end
35              C: begin
36                  if (~w) Y_D = E;
37                  else Y_D = D;
38              end
39              D: begin
40                  if (~w) Y_D = E;
41                  else Y_D = F;
42              end
43              E: begin
44                  if (~w) Y_D = A;
45                  else Y_D = G;
46              end
47              F: begin
48                  if (~w) Y_D = E;
49                  else Y_D = F;
50              end
51              G: begin
52                  if (~w) Y_D = A;
53                  else Y_D = C;
54              end
55              default: Y_D = A;
56          endcase
57
58      end // state_table
59
60      // state Registers
61      always @(posedge clock)
62      begin: state_FFS
63          if(resetn == 1'b0)
64              y_Q <= A; // reset to state A
65          else
66              y_Q <= Y_D;
67      end // state_FFS
68
69      // output logic
70      assign out_light = ((y_Q == F) | (y_Q == G));
71
72      assign LEDR[9] = out_light;
73      assign LEDR[3:0] = y_Q;
74      assign LEDR[8:4] = 5'd0;
75
76  endmodule // sequence_detector

```



```

1  `timescale 1ns / 1ns // `timescale time_unit/time_precision
2
3  /* top-level entity for polynomial calculator */
4  module fpga_top (input [9:0] SW, input [3:0] KEY, input CLOCK_50,
5                  output [9:0] LEDR, output [6:0] HEX0, HEX1);
6
7      wire resetn;
8      wire go;
9      wire [7:0] data_result;
10
11     /*
12      * SW[7:0] is data_in
13      * KEY[0] synchronous reset when pressed
14      * KEY[1] is go signal
15      * LEDR displays result
16      * HEX0 and HEX1 also display result
17     */
18
19     assign go = ~KEY[1];
20     assign resetn = KEY[0];
21     assign LEDR[7:0] = data_result;
22
23     poly_calc u0 (.clk(CLOCK_50), .resetn(resetn), .go(go), .data_in(SW[7:0]),
24                 .data_result(data_result));
25     hex_decoder H0 (.hex_digit(data_result[3:0]), .segments(HEX0));
26     hex_decoder H1 (.hex_digit(data_result[7:4]), .segments(HEX1));
27
28 endmodule // fpga_top
29
30 /* polynomial calculator */
31 module poly_calc (input clk, resetn, go, input [7:0] data_in,
32                  output [7:0] data_result);
33
34     // wires to connect datapath and control
35     wire ld_a, ld_b, ld_c, ld_x, ld_r;
36     wire ld_alu_out;
37     wire [1:0] alu_select_a, alu_select_b;
38     wire alu_op;
39
40     control C0 (.clk(clk), .resetn(resetn), .go(go), .ld_alu_out(ld_alu_out),
41                .ld_x(ld_x), .ld_a(ld_a), .ld_b(ld_b), .ld_c(ld_c),
42                .ld_r(ld_r), .alu_select_a(alu_select_a),
43                .alu_select_b(alu_select_b), .alu_op(alu_op));
44
45     datapath D0 (.clk(clk), .resetn(resetn), .ld_alu_out(ld_alu_out),
46                 .ld_x(ld_x), .ld_a(ld_a), .ld_b(ld_b), .ld_c(ld_c),
47                 .ld_r(ld_r), .alu_select_a(alu_select_a),
48                 .alu_select_b(alu_select_b), .alu_op(alu_op),
49                 .data_in(data_in), .data_result(data_result));
50
51 endmodule // poly_calc
52
53 /* controls registers and state transition */
54 module control (input clk, resetn, go, output reg ld_a, ld_b, ld_c, ld_x,
55                ld_r, ld_alu_out, output reg [1:0] alu_select_a, alu_select_b,
56                output reg alu_op);
57
58     reg [5:0] current_state, next_state;
59     localparam S_LOAD_A = 5'd0,
60                S_LOAD_A_WAIT = 5'd1,
61                S_LOAD_B = 5'd2,
62                S_LOAD_B_WAIT = 5'd3,
63                S_LOAD_C = 5'd4,
64                S_LOAD_C_WAIT = 5'd5,
65                S_LOAD_X = 5'd6,
66                S_LOAD_X_WAIT = 5'd7,
67                S_CYCLE_0 = 5'd8,
68                S_CYCLE_1 = 5'd9,
69                S_CYCLE_2 = 5'd10,
70                S_CYCLE_3 = 5'd11;
71
72     // state table
73     always @(*)
74     begin
75         case (current_state)
76             // loop in current state until value is input

```

```

77     S_LOAD_A: next_state = go ? S_LOAD_A_WAIT : S_LOAD_A;
78     // loop in current state until go signal goes low
79     S_LOAD_A_WAIT: next_state = go ? S_LOAD_A_WAIT : S_LOAD_B;
80     // loop in current state until value is input
81     S_LOAD_B: next_state = go ? S_LOAD_B_WAIT : S_LOAD_B;
82     // loop in current state until go signal goes low
83     S_LOAD_B_WAIT: next_state = go ? S_LOAD_B_WAIT : S_LOAD_C;
84     // loop in current state until value is input
85     S_LOAD_C: next_state = go ? S_LOAD_C_WAIT : S_LOAD_C;
86     // loop in current state until go signal goes low
87     S_LOAD_C_WAIT: next_state = go ? S_LOAD_C_WAIT : S_LOAD_X;
88     // loop in current state until value is input
89     S_LOAD_X: next_state = go ? S_LOAD_X_WAIT : S_LOAD_X;
90     // loop in current state until go signal goes low
91     S_LOAD_X_WAIT: next_state = go ? S_LOAD_X_WAIT : S_CYCLE_0;
92     S_CYCLE_0: next_state = S_CYCLE_1;
93     S_CYCLE_1: next_state = S_CYCLE_2;
94     S_CYCLE_2: next_state = S_CYCLE_3;
95     // start over after
96     S_CYCLE_3: next_state = S_LOAD_A;
97     default: next_state = S_LOAD_A;
98 endcase
99
100 end // state_table
101
102
103 // output logic for datapath control signals
104 always @(*)
105 begin
106     // all signals are 0 by default, to avoid latches.
107
108     ld_alu_out = 1'b0;
109     ld_a = 1'b0;
110     ld_b = 1'b0;
111     ld_c = 1'b0;
112     ld_x = 1'b0;
113     ld_r = 1'b0;
114     alu_select_a = 2'b0;
115     alu_select_b = 2'b0;
116     alu_op = 1'b0;
117
118     case (current_state)
119     S_LOAD_A: begin
120         ld_a = 1'b1;
121     end
122     S_LOAD_B: begin
123         ld_b = 1'b1;
124     end
125     S_LOAD_C: begin
126         ld_c = 1'b1;
127     end
128     S_LOAD_X: begin
129         ld_x = 1'b1;
130     end
131     S_CYCLE_0: begin // do B <- B * x
132         ld_alu_out = 1'b1; ld_b = 1'b1; // store result back into B
133         alu_select_a = 2'd1; // select register B
134         alu_select_b = 2'd3; // also select register x
135         alu_op = 1'b1; // do multiply operation
136     end
137     S_CYCLE_1: begin // do A <- A + B
138         ld_alu_out = 1'b1; ld_a = 1'b1; // store result back into A
139         alu_select_a = 2'd0; // select register A
140         alu_select_b = 2'd1; // also select register B
141         alu_op = 1'b0; // do addition operation
142     end
143     S_CYCLE_2: begin // do A <- A * x
144         ld_alu_out = 1'b1; ld_a = 1'b1; // store result back into A
145         alu_select_a = 2'd0; // select register A
146         alu_select_b = 2'd3; // also select register x
147         alu_op = 1'b1; // do multiply operation
148     end
149     S_CYCLE_3: begin // do A + C
150         ld_r = 1'b1; // store result in result register
151         alu_select_a = 2'd0; // select register A
152         alu_select_b = 2'd2; // select register C

```

```

153             alu_op = 1'b0; // do addition operation
154         end
155         // no default needed; all of our outputs were assigned a value
156     endcase
157 end // enable_signals
158
159 // current_state registers
160 always @(posedge clk)
161 begin
162     if(!resetn)
163         current_state <= S_LOAD_A;
164     else
165         current_state <= next_state;
166     end // state_FFS
167 endmodule // control
168
169 module datapath (input clk, resetn, ld_x, ld_a, ld_b, ld_c,
170                 ld_r, alu_op, ld_alu_out, input [7:0] data_in,
171                 input [1:0] alu_select_a, alu_select_b,
172                 output reg [7:0] data_result);
173
174     reg [7:0] a, b, c, x; // input registers
175     reg [7:0] alu_out; // output of the alu
176     reg [7:0] alu_a, alu_b; // alu input muxes
177
178     // registers a, b, c, x with respective input logic
179     always@(posedge clk) begin
180         if(!resetn)
181         begin
182             a <= 8'b0;
183             b <= 8'b0;
184             c <= 8'b0;
185             x <= 8'b0;
186         end
187
188         else
189         begin
190             // load alu_out if load_alu_out signal is high, otherwise load from data_in
191             if(ld_a)
192                 a <= ld_alu_out ? alu_out : data_in;
193             // load alu_out if load_alu_out signal is high, otherwise load from data_in
194             if(ld_b)
195                 b <= ld_alu_out ? alu_out : data_in;
196             if(ld_x)
197                 x <= data_in;
198             if(ld_c)
199                 c <= data_in;
200         end
201     end
202
203     // output result register
204     always@(posedge clk) begin
205         if(!resetn) begin
206             data_result <= 8'b0;
207         end
208         else
209         begin
210             if(ld_r)
211                 data_result <= alu_out;
212         end
213     end
214
215     // the ALU input multiplexers
216     always @(*)
217     begin
218         case (alu_select_a)
219             2'd0:
220                 alu_a = a;
221             2'd1:
222                 alu_a = b;
223             2'd2:
224                 alu_a = c;
225             2'd3:
226                 alu_a = x;
227             default: alu_a = 8'b0;
228         endcase

```

```

229         endcase
230
231     case (alu_select_b)
232         2'd0:
233             alu_b = a;
234         2'd1:
235             alu_b = b;
236         2'd2:
237             alu_b = c;
238         2'd3:
239             alu_b = x;
240         default: alu_b = 8'b0;
241     endcase
242 end
243
244 // ALU
245 always @(*)
246 begin : ALU
247     case (alu_op)
248         // performs addition
249         0: begin
250             alu_out = alu_a + alu_b;
251         end
252         // performs multiplication
253         1: begin
254             alu_out = alu_a * alu_b;
255         end
256         default: alu_out = 8'b0;
257     endcase
258 end
259
260 endmodule // datapath
261
262 /* bcd to hex for seven-segment display */
263 module hex_decoder(input [3:0] hex_digit, output reg [6:0] segments);
264
265     always @(*)
266     begin
267
268         case (hex_digit)
269             4'h0: segments = 7'b100_0000;
270             4'h1: segments = 7'b111_1001;
271             4'h2: segments = 7'b010_0100;
272             4'h3: segments = 7'b011_0000;
273             4'h4: segments = 7'b001_1001;
274             4'h5: segments = 7'b001_0010;
275             4'h6: segments = 7'b000_0010;
276             4'h7: segments = 7'b111_1000;
277             4'h8: segments = 7'b000_0000;
278             4'h9: segments = 7'b001_1000;
279             4'hA: segments = 7'b000_1000;
280             4'hB: segments = 7'b000_0011;
281             4'hC: segments = 7'b100_0110;
282             4'hD: segments = 7'b010_0001;
283             4'hE: segments = 7'b000_0110;
284             4'hF: segments = 7'b000_1110;
285             default: segments = 7'h7f;
286         endcase
287
288     end
289
290 endmodule // hex_decoder

```

